

Converter Design_Ass6

AA1505 - M.T. Ahamed
 AA1375 - Pasindu Charuka
 AA2127 - B.D.R Fernando
 AA1465 - Dulan hettiorachchi
 AA1483 - S.T. Salinda Prabath Pasindu

Group
 Assignment - 06

Task 1

Index - AA1505
 XYZ

Consider 0 as 5

X, Y, Z = 5

$$V_{in} = (X + Z/10) V \pm 10\%$$

$$V_{in} = (5 + \frac{5}{10}) \pm 10\% \rightarrow V_{in(max)} = 6.05V$$

$$V_{in(min)} = 4.95V$$

$$= 5.5 \pm 10\%$$

$$\text{Load current} = 50 \times 2 \text{ mA}$$

$$= 250 \text{ mA}$$

$$V_{out} = 16.5 \pm 10\%$$

$$\text{Switching freq} = 100 \text{ kHz}$$

$$\frac{T_{on}}{T_{off}} = \frac{V_{out} + V_F - V_{in(min)}}{V_{in(min)} - V_{sat}} = \frac{16.5 + 0.4 - 4.95}{4.95 - 0.5} = \frac{11.95}{4.45} = 2.43 //$$

$$T_{on} + T_{off} = \frac{1}{f} = \frac{1}{100 \text{ kHz}} = 10 \mu s$$

$$T_{off} = \left(\frac{T_{on} + T_{off}}{\left(\frac{T_{on}}{T_{off}} \right) + 1} \right) = \frac{10 \mu s}{2.43 + 1} = 2.91 \mu s$$

$$T_{on} = (T_{on} + T_{off}) - T_{off} = 10 \mu s - 2.91 \mu s = 7.09 \mu s$$

$$C_T = 4.0 \times 10^{-5} \times T_{ON} = 4 \times 10^{-5} \times 7.09 \mu s = \underline{\underline{283 \text{ PF}}}$$

$$I_{peak} = 2 \times I_{cut \max} \left[\frac{T_{ON}}{T_{OFF}} + 1 \right] = 2 \times 0.25 \left[\frac{2.93}{1} + 1 \right] = \underline{\underline{1.715 \text{ A}}}$$

$$R_{sc} = \frac{0.3}{I_P} = \frac{0.3}{1.715} = 0.174 \Omega$$

$$L_{min} = \left(\frac{V_{in(min)} - V_{sat}}{I_{peak}} \right) \times T_{ON} = \left(\frac{4.95 - 0.5}{1.715} \right) \times 7.09 = \underline{\underline{20 \mu H}}$$

$$C_{out} = \frac{9 \times I_{cut} \times T_{ON}}{V_{ripple}} = \frac{9 \times 0.25 \times 7.09}{0.1} = 159.5 \mu F$$

Feedback R value

$$V_{out} = 1.25 \left(1 + \frac{R_2}{R_1} \right)$$

$$R_2 = \frac{V_{out}}{1.25} - 1 \times R_1$$

IF $R_1 = 10K$

$$R_2 = \frac{16.5}{1.25} - 1 \times 10 \times 10^3$$

$$R_2 = 118K$$

No. _____ Date: ____/____/____

4) Safety margins

MIN Input Voltage.

MIN Startup Voltage. at Load.

Shutdown Current.

Noise

5) RMS current of the input capacitor C_{in} can be calculated by

$$I_{Cin, RMS} = I_{out} \times \sqrt{D - D^2} \quad ; D - \text{PWM square wave duty cycle.}$$

The worst case occurs at $D = 50\%$.

$$V_{in} = 2 \times V_{out}$$

$$I_{in, RMS} = I_{out} / 2$$

7) NO. Exactly NOT matching.

8) 4 wire sensing method is an electrical impedance measuring technique that uses separate pairs of current-carrying and voltage-sensing electrodes to make more accurate measurements than the simpler and more usual two-terminal sensing.

9) Power dissipated in a resistor given by $P = V^2/R$ which means power decreases if resistance increases.

The power also given by $P = I^2 R$; which means power increases if resistance increases.

10) Affecting factors are,

Temperature

Length of wire.

Area of cross section of wire.

increases resistance.

No: _____

Date: ____/____/____

4


decrease the length of wire.

Use small cross section Area wire.

Task 2


Line Regulation.

$V_{in}(V)$	$I_1 = 500mA$ V_{out}	$I_2 = 1A$ V_{out}	$I_3 = 1.5A$ V_{out}
5	0.37	0.21	0.2
10	3.60	3.5	0.8
15	6.64	4.31	0.82
20	9.78	4.30	0.73
25	13.00	3.9	0.72

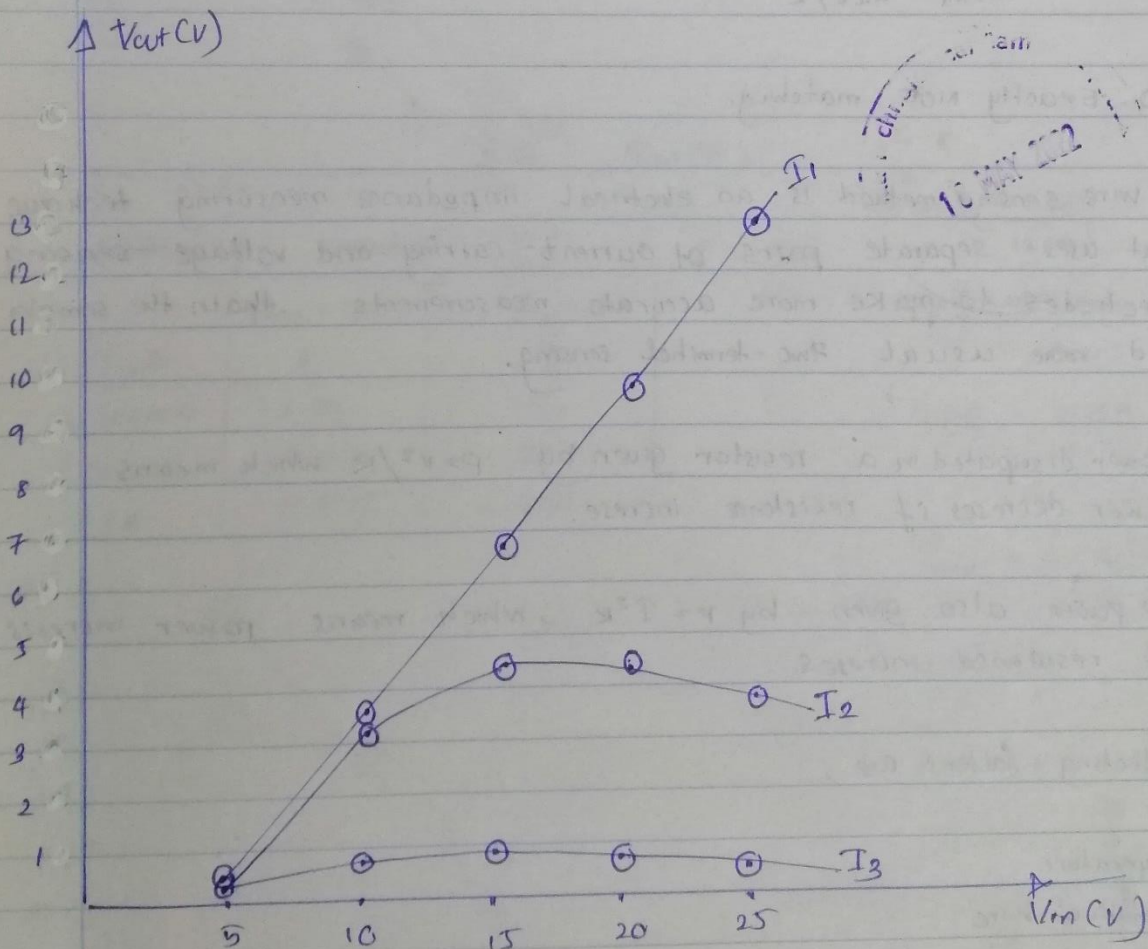

No: _____ Date: ____/____/____ Load Regulation

	$V_{in1} = 12V$	$V_{in2} = 15V$	$V_{in3} = 18V$
I_{out}	V_{out}	V_{out}	V_{out}
0	15	15	15
500 mA	9	8.3	9.31
1 A	7.1	7.21	5.1
1.5 A	3.2	1.2	0.76

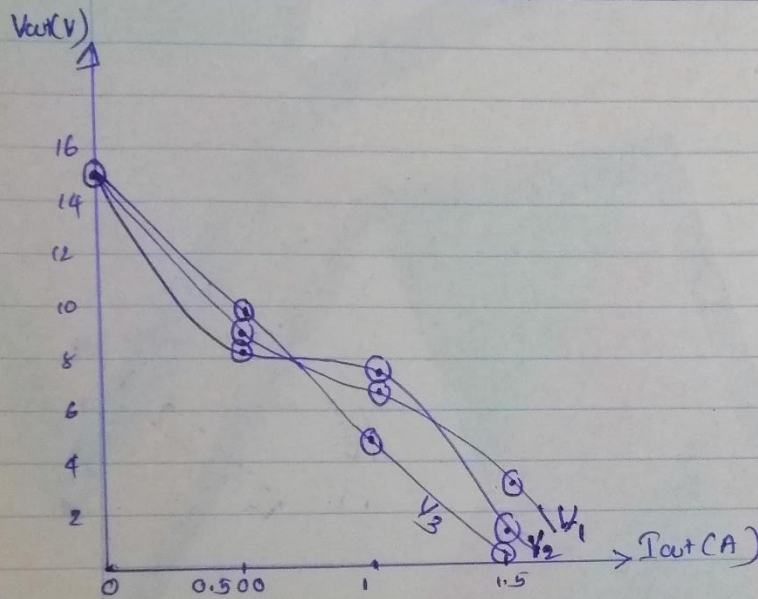

Efficiency Variation (η)

	$V_{in1} = 12V$	$V_{in2} = 18V$
I_{out}	η	η
100 mA	1.93	1.3
500 mA	1.206	1.297
1 A	0.7125	0.471

$$\eta = \frac{P_{out}}{P_{in}}$$

$$\frac{12V}{100mA} \eta = \frac{2.34W}{12 \times 0.1} = 1.93$$


$$\frac{18V}{500mA} \eta = \frac{7.29W}{18 \times 0.5} = 1.206$$

$$1A \eta = \frac{8.55W}{12 \times 1} = 0.7125$$

$$\frac{18V}{100mA} \eta = \frac{2.34W}{18 \times 0.1} = 1.3$$

$$\frac{18V}{500mA} \eta = \frac{11.68W}{18 \times 0.5} = 1.297$$

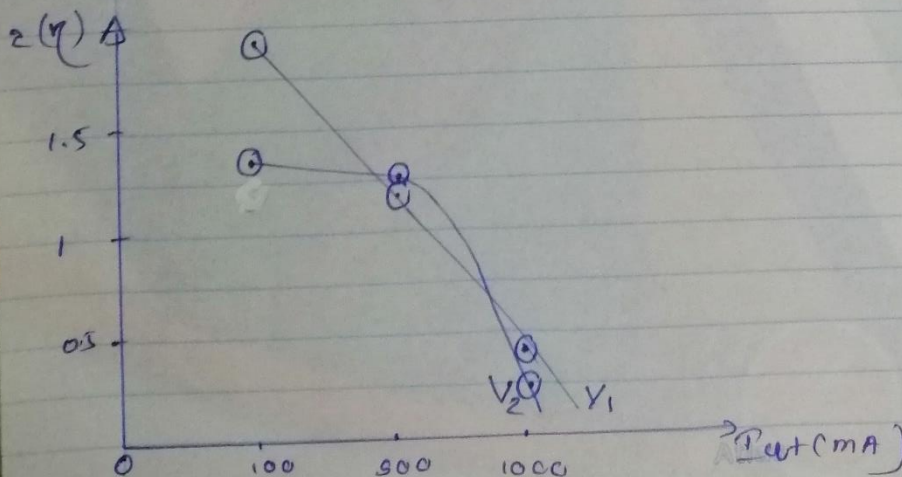
$$1A \eta = \frac{8.48W}{18 \times 1} = 0.471$$




No: 123

Date: / /


Output ripple variation

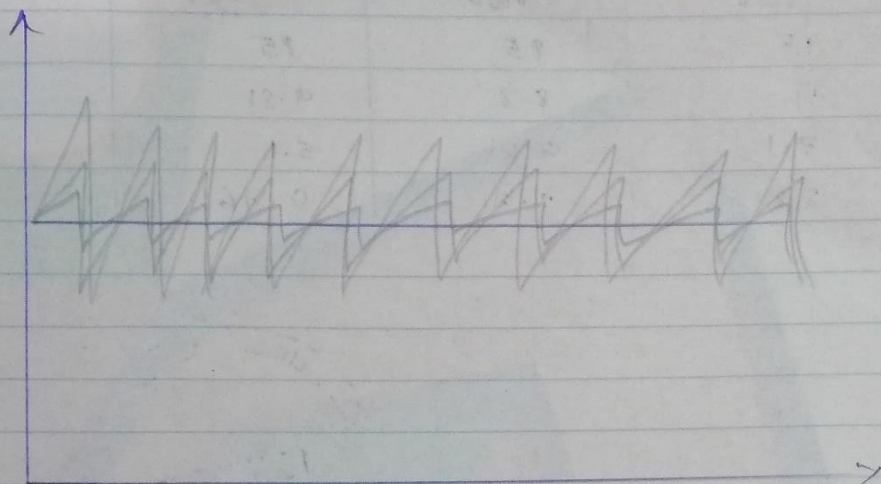


classmate
10 MAY 12

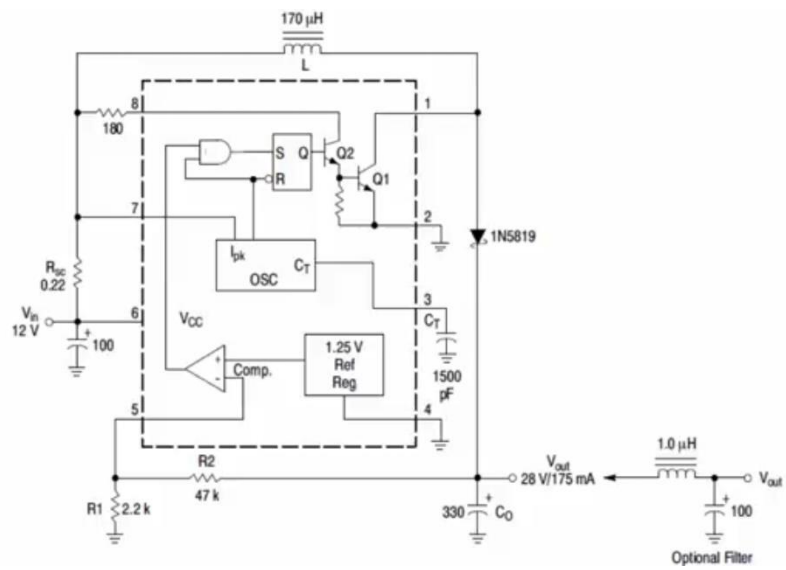


Circuit Diagram


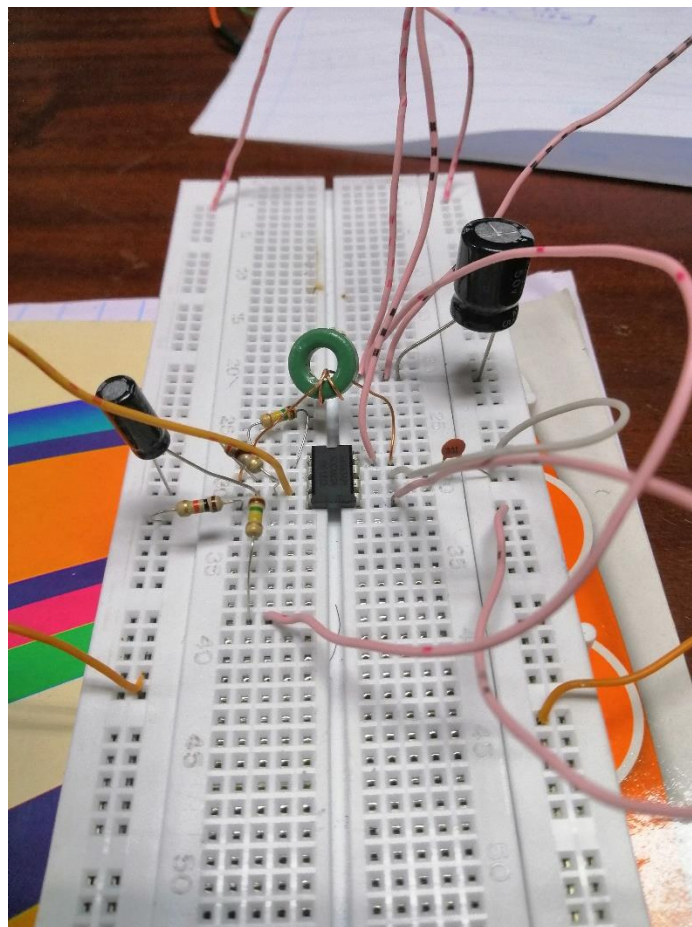


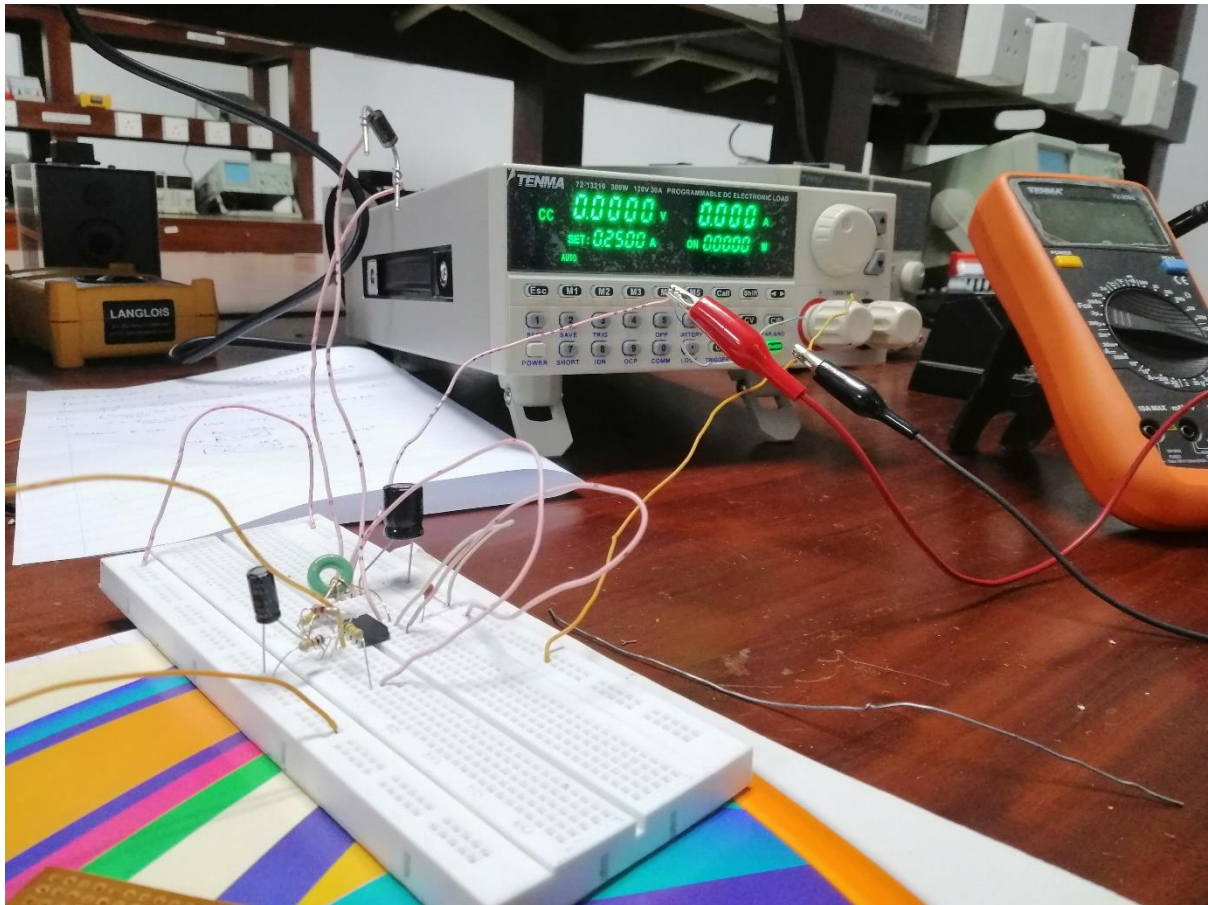


Breadboard implementation

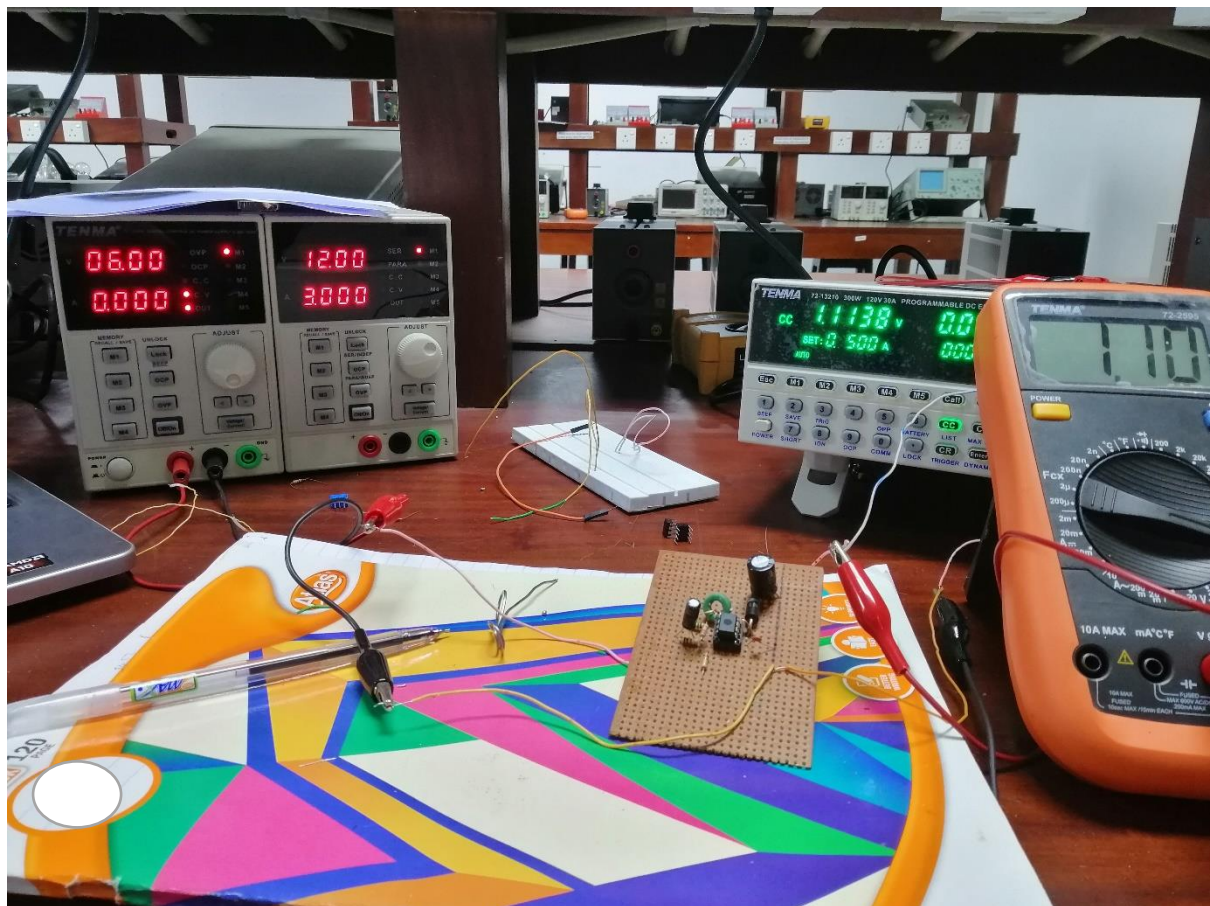



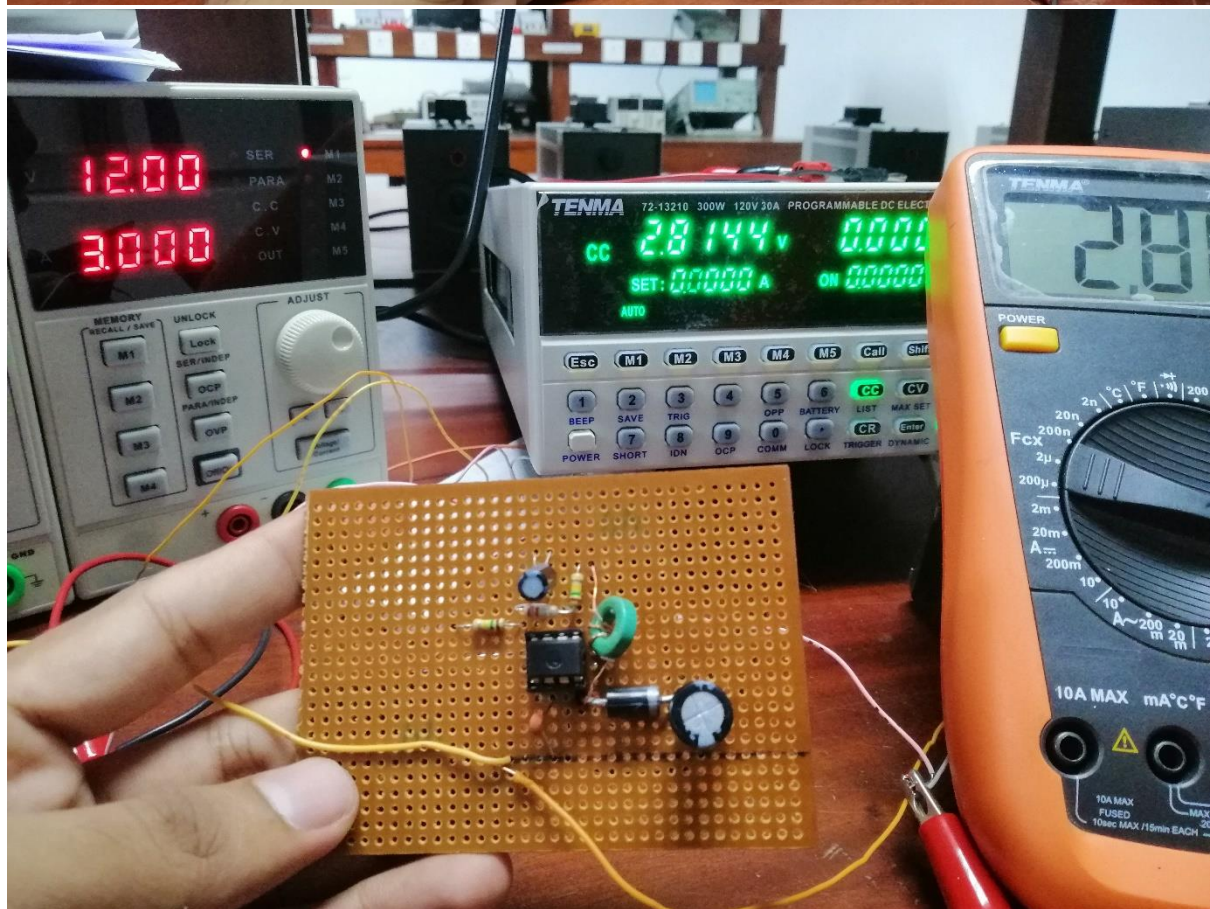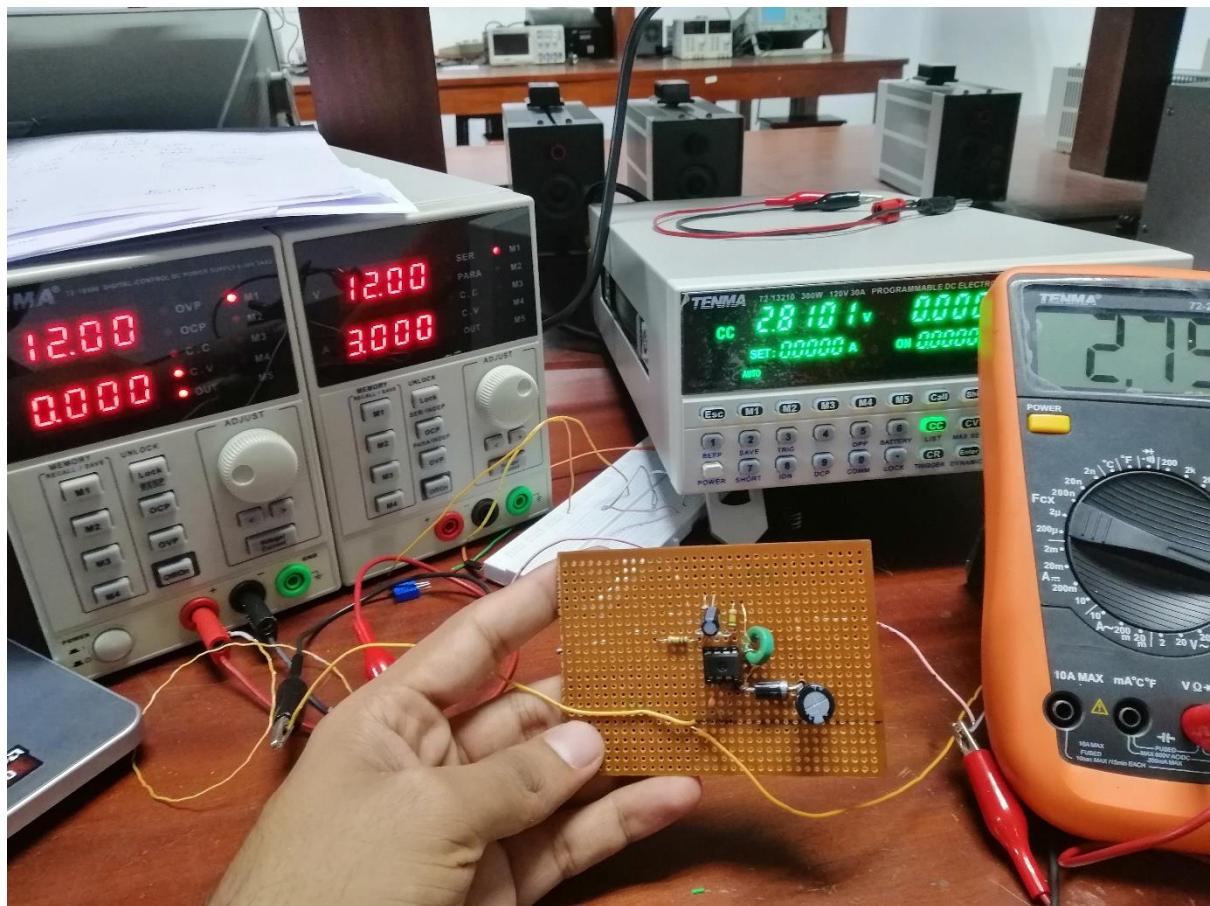

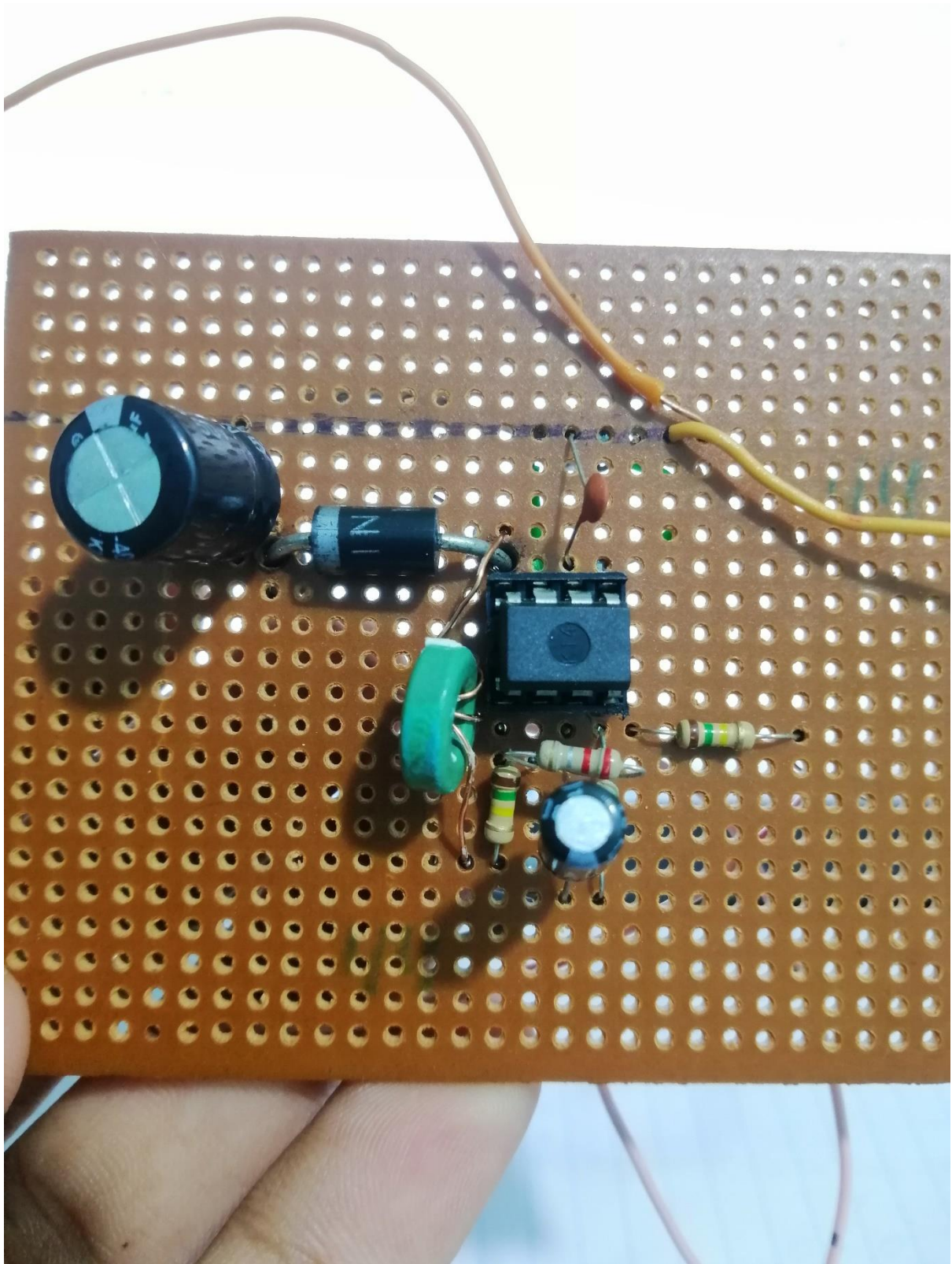

Converter Circuit